

# GATE 2023 PH Q37

EE23BTECH11009 - AROSHISH PRADHAN\*

**Question:** In the circuit shown below, the switch S is closed at  $t = 0$ . The magnitude of the steady state voltage, in volts, across the  $6\Omega$  resistor is \_\_\_\_\_.(round off to two decimal places)

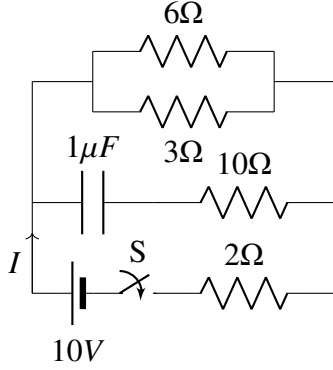


Fig. 1

Using KCL and KVL, we can calculate:

$$Z_{\text{eff}} = \frac{2\left(10 + \frac{1}{j\omega C}\right)}{12 + \frac{1}{j\omega C}} + 2 \quad (1)$$

$$\Rightarrow I(j\omega) = \frac{V_{in}}{\left(\frac{2\left(10 + \frac{1}{j\omega C}\right)}{12 + \frac{1}{j\omega C}} + 2\right)} \quad (2)$$

$$\Rightarrow V_{out}(j\omega) = 2 \left[ \left( \frac{10 + \frac{1}{j\omega C}}{12 + \frac{1}{j\omega C}} \right) I(j\omega) \right] \quad (3)$$

$$= 2 \left[ \left( \frac{10 + \frac{1}{j\omega C}}{12 + \frac{1}{j\omega C}} \right) \frac{V_{in}(j\omega)}{\left( \frac{2\left(10 + \frac{1}{j\omega C}\right)}{12 + \frac{1}{j\omega C}} + 2 \right)} \right] \quad (4)$$

$$\Rightarrow H(j\omega) = \frac{1 + 10j\omega C}{2(1 + 11j\omega C)} \quad (5)$$

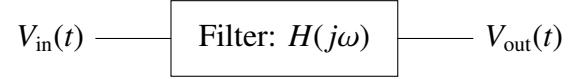


Fig. 2: Filter Equivalent of Circuit

$$H(j\omega) = \left( \frac{\sqrt{1 + 100\omega^2 C^2}}{2\sqrt{1 + 121\omega^2 C^2}} \right) e^{j(\tan^{-1}(10\omega C) - \tan^{-1}(11\omega C))} \quad (6)$$

$$= \left( \frac{\sqrt{1 + 100\omega^2 C^2}}{2\sqrt{1 + 121\omega^2 C^2}} \right) e^{j \tan^{-1}\left(\frac{-\omega C}{1 + 110\omega^2 C^2}\right)} \quad (7)$$

$$\therefore V_{out}(t) = 10 |H(j\omega)| \cos(\omega t + \angle H(j\omega)) \quad (8)$$

$$= \frac{5\sqrt{1 + 100\omega^2 C^2}}{\sqrt{1 + 121\omega^2 C^2}} \cos\left(\omega t - \tan^{-1}\left(\frac{\omega C}{1 + 110\omega^2 C^2}\right)\right) \quad (9)$$

**Solution:** Consider a sinusoidal input source of angular frequency  $\omega$ .

Symbol	Value	Description
$\omega$	0 for D.C.	Angular Frequency
$C$	$1\mu F$	Capacitance
$V_{in}(t)$	$10 \cos(\omega t)$	Input Voltage
$V_{out}(t)$		Output Voltage across $6\Omega$
$V_{out}(j\omega)$	$H(j\omega)V_{in}(j\omega)$	Output in Frequency Domain
$H(j\omega)$		Transfer Function
$I(j\omega)$		Total Current
$Z_{\text{eff}}$		Overall Impedance

TABLE I: Given Parameters

As  $\omega \rightarrow 0$ ,  $V_{in}(t)$  approaches being a D.C. input source (10V).

$\therefore$  substituting  $\omega = 0$ , we get:

$$V_{out}(t) = 5V \quad (10)$$

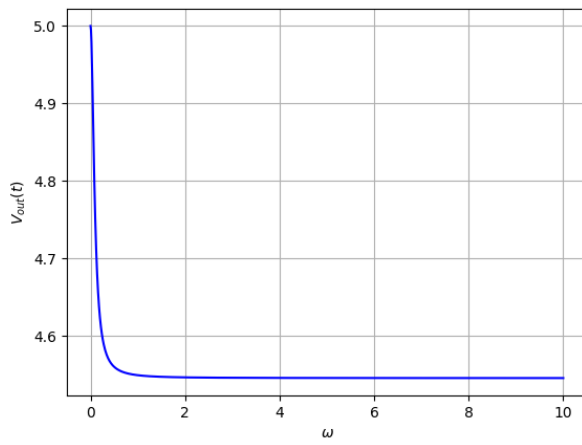


Fig. 3: Plot of  $V_{out}(t)$  at  $t = 0$  w.r.t  $\omega$