

GATE 22 IN/63

EE23BTECH11040 - Manoj Kumar Ambatipudi*

QUESTION: The bridge shown is balanced when $R_1 = 100\Omega$, $R_2 = 210\Omega$, $C_2 = 2.9\mu F$, $R_4 = 50\Omega$. The 2kHz sine-wave generator supplies a voltage of $10V_{p-p}$. The value of L_3 (in mH) is?

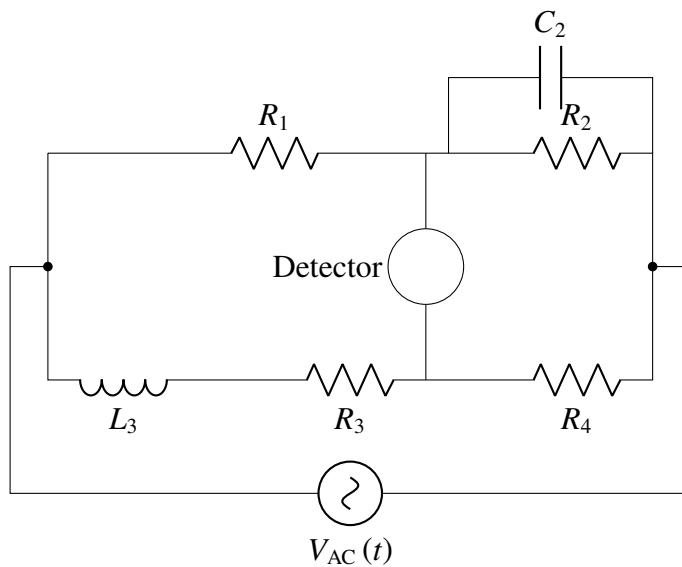


Fig. 1. Circuit in T domain

Solution:

Variables	Description	value
R_1	Resistor 1	100Ω
R_2	Resistor 2	210Ω
R_3	Resistor 3	?
R_4	Resistor 4	50Ω
C_2	Capacitor 2	$2.9\mu F$
L_3	Inductor 3	?

TABLE 1
CAPTION

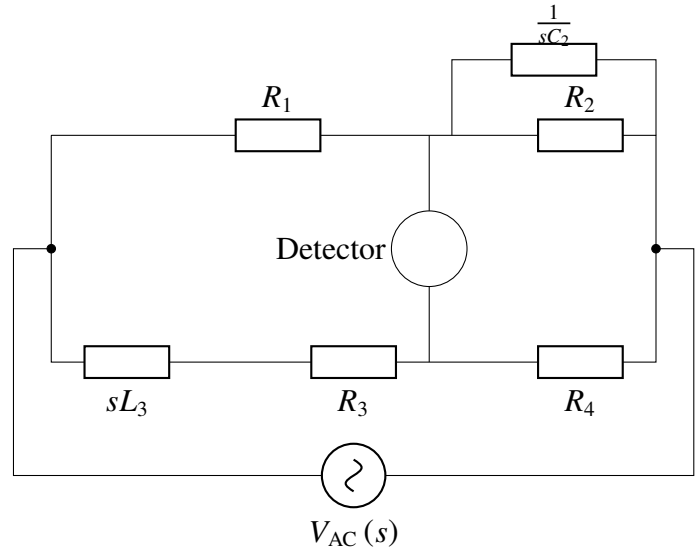


Fig. 2. Circuit in S domain

Applying Wheatstone bridge condition,

$$\frac{R_1}{sL_3 + R_3} = \frac{\frac{1}{\frac{1}{R_2} + sC_2}}{R_4} \quad (1)$$

$$\Rightarrow \frac{R_1}{sL_3 + R_3} = \frac{1}{\left(\frac{1}{R_2} + sC_2\right) R_4} \quad (2)$$

$$\Rightarrow \frac{sL_3 + R_3}{R_1} = \left(\frac{1}{R_2} + sC_2\right) R_4 \quad (3)$$

$$\Rightarrow \frac{sL_3}{R_1} + \frac{R_3}{R_1} = \frac{R_4}{R_2} + sC_2 R_4 \quad (4)$$

Comparing coefficients, we get

$$\frac{L_3}{R_1} = C_2 R_4 \quad (5)$$

$$\Rightarrow L_3 = R_1 C_2 R_4 \quad (6)$$

$$\frac{R_3}{R_1} = \frac{R_4}{R_2} \quad (7)$$

$$\Rightarrow R_3 = \frac{R_1 R_4}{R_2} \quad (8)$$

From Table 1, substituting in (6) and (8), we get

$$L_3 = 14.5mH \quad (9)$$

$$R_3 = 23.80\Omega \quad (10)$$

The circuit in S domain is