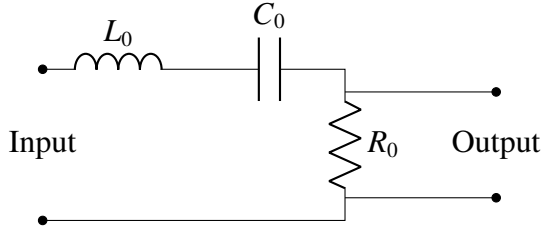


GATE 22 IN/33

EE23BTECH11040 - Manoj Kumar Ambatipudi*

QUESTION: In the bandpass filter circuit shown, $R_0 = 50\Omega$, $L_0 = 1mH$, $C_0 = 10nF$. The q factor of the filter is




SOLUTION:

Variable	Description	Value
R_0	Resistance	50Ω
L_0	Inductance	$1mH$
C_0	Capacitance	$10nF$
ω_0	Resonant Angular Frequency	$\frac{1}{\sqrt{L_0 C_0}}$

TABLE 1

VARIABLES AND THEIR DESCRIPTION

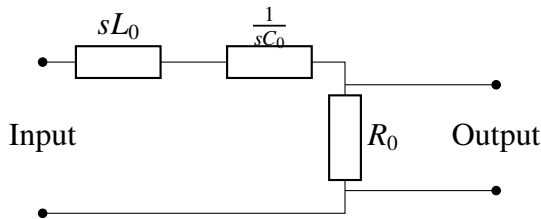The corresponding Laplace domain circuit is



Input $X(s)$ can be written as

$$X(s) = I(s) \left(sL_0 + \frac{1}{sC_0} + R_0 \right) \quad (1)$$

Output $Y(s)$ can be written as

$$Y(s) = I(s) R_0 \quad (2)$$

Transfer function $H(s)$ can be written as

$$H(s) = \frac{Y(s)}{X(s)} \quad (3)$$

$$= \frac{sC_0 R_0}{s^2 C_0 L_0 + C_0 R_0 s + 1} \quad (4)$$

substituting $s = j\omega$

$$H(j, \omega) = \frac{j\omega C_0 R_0}{-\omega^2 C_0 L_0 + jC_0 R_0 \omega + 1} \quad (5)$$

$$\Rightarrow |H(j, \omega)| = \frac{\omega C_0 R_0}{\sqrt{(1 - \omega^2 C_0 L_0)^2 + (C_0 R_0 \omega)^2}} \quad (6)$$

Differentiating w.r.t ω and equating to 0, we get

$$\frac{d|H(j, \omega)|}{d\omega} = \frac{C_0 R_0}{\sqrt{(1 - \omega^2 C_0 L_0)^2 + (C_0 R_0 \omega)^2}} + \frac{\omega C_0 R_0}{2 \left((1 - \omega^2 C_0 L_0)^2 + (C_0 R_0 \omega)^2 \right)^{\frac{3}{2}}} \left(2\omega (C_0 R_0)^2 - 2(1 - \omega^2 C_0 L_0) 2\omega \right) = 0 \quad (7)$$

$$\Rightarrow \omega_0 = \frac{1}{\sqrt{L_0 C_0}} \quad (8)$$

from Table 1,

$$\omega_0 = 316227.76 \quad (9)$$

Q - factor defined with reference to inductor

$$Q = \left| \frac{V_L}{V_R} \right|_{\omega_0} \quad (10)$$

$$= \frac{L_0 \omega_0}{R_0} \quad (11)$$

$$= \frac{1}{R_0} \sqrt{\frac{L_0}{C_0}} \quad (\text{from (8)}) \quad (12)$$

Q - factor defined with reference to capacitor

$$Q = \left| \frac{V_C}{V_R} \right|_{\omega_0} \quad (13)$$

$$= \frac{1}{C_0 \omega_0 R_0} \quad (14)$$

$$= \frac{1}{R_0} \sqrt{\frac{L_0}{C_0}} \quad (\text{from (8)}) \quad (15)$$

(3) Substituting the values from Table 1, we get

$$Q = 200 \quad (16)$$

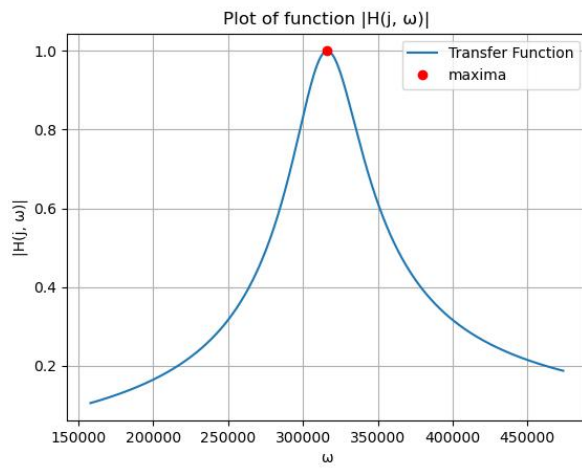


Fig. 1. Transfer function $|H(j, \omega)|$ taken from python3