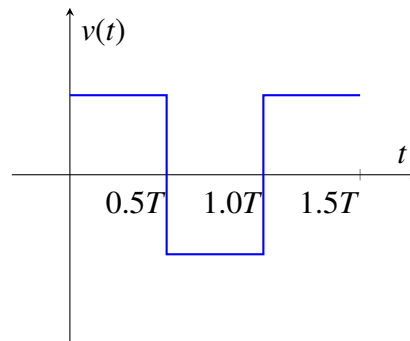


Gate-2022-EE-58

EE22BTECH11008 - Annapureddy Siva Meenakshi*

Q: Consider an ideal full-bridge single-phase DC-AC inverter with a DC bus voltage magnitude of 1000V. The inverter output voltage $v(t)$ shown below is obtained when diagonal switches of the inverter are switched with 50% duty cycle. The inverter feeds a load with a sinusoidal current given by $i(t) = 10 \sin(\omega t - \frac{\pi}{3})$ A, where $\omega = \frac{2\pi}{T}$. The active power, in watts, delivered to the load is __.[Gate2022-EE-58]



Solution:

Variable	Description	Value
V_s	input DC voltage	1000V
$i(t)$	output current	$\sin(\omega t - \frac{\pi}{3})$
$v(t)$	Output voltage	given
ω	Frequency	$\frac{2\pi}{T}$
v_0^{rms}	RMS output voltage at the fundamental frequency	none
i_{rms}	RMS output current at the fundamental frequency	none
$v_0(t)$	output voltage at the fundamental frequency	none
ϕ	phase difference between $v_0(t)$ and $i(t)$	none
i_0	amplitude of output current	1
P	active power delivered	none

TABLE 0: Input parameters

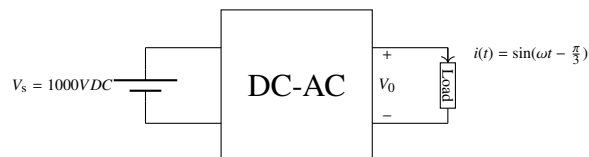


Fig. 0: circuit diagram of the system

The Fourier series expansion of the given voltage $v(t)$ is,

$$v(t) = \sum_{n=1,3,5,\dots}^{\infty} \frac{4V_{dc}}{n\pi} \sin(n\omega t) \quad (1)$$

$$v_0(t) = \frac{4V_{dc}}{\pi} \sin(\omega t) \quad (2)$$

$$\therefore \phi = \frac{\pi}{3} \quad (3)$$

$$v_0^{rms} = \frac{4V_{dc}}{\pi \sqrt{2}} \quad (4)$$

$$= \frac{4000}{\pi \sqrt{2}} \quad (5)$$

$$i_{rms} = \frac{i_0}{\sqrt{2}} = \frac{1}{\sqrt{2}} \quad (6)$$

Active power delivered to load in Watts is given by,

$$P = v_0^{rms} \times i_{rms} \times \cos \phi \quad (7)$$

$$= \frac{4000}{\pi \sqrt{2}} \times \frac{1}{\sqrt{2}} \times \cos \frac{\pi}{3} \quad (8)$$

$$\approx 3183 \quad (9)$$

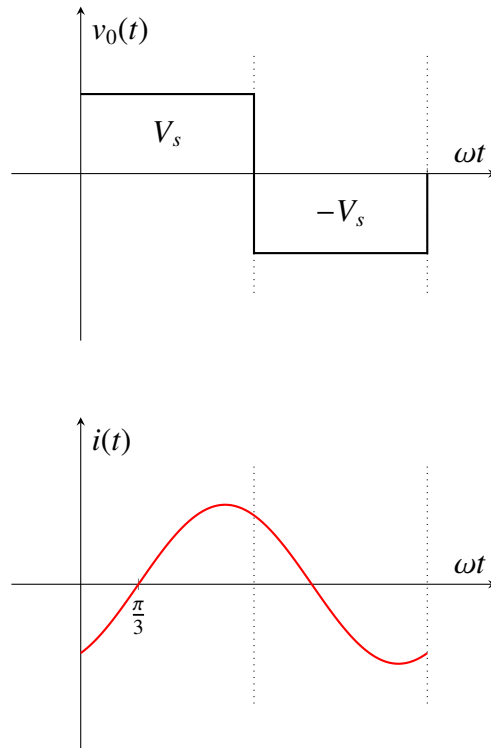


Fig. 0: output voltage and current of the system