

## EE23BTECH11047 - Deepakreddy P

**32** A single-phase full-bridge diode rectifier feeds a resistive load of  $50\Omega$  from a  $200\text{ V}$ ,  $50\text{ Hz}$  single phase AC supply. If the diodes are ideal, then the active power, in watts, drawn by the load is \_\_\_\_\_ (round off to nearest integer).  
(GATE EE 32)

**Solution:**

Table I  
INPUT PARAMETERS

Symbol	Description	value
R	Load Resistance	$50\Omega$
$V_{rms}$	RMS Voltage	$200\text{V}$
f	Frequency	$50\text{Hz}$

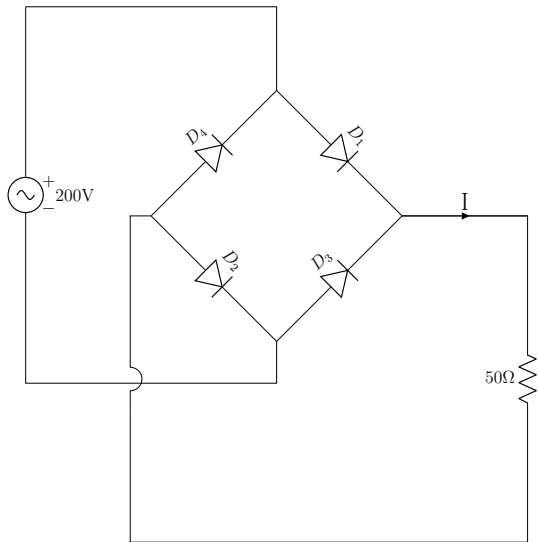


Figure 1. Circuit-1

$$V_{rms} = 200 \quad (1)$$

$$P = \frac{(V_{rms})^2}{R} \quad (2)$$

$$P = \frac{(200)^2}{50} W \quad (3)$$

$$P = 800W \quad (4)$$

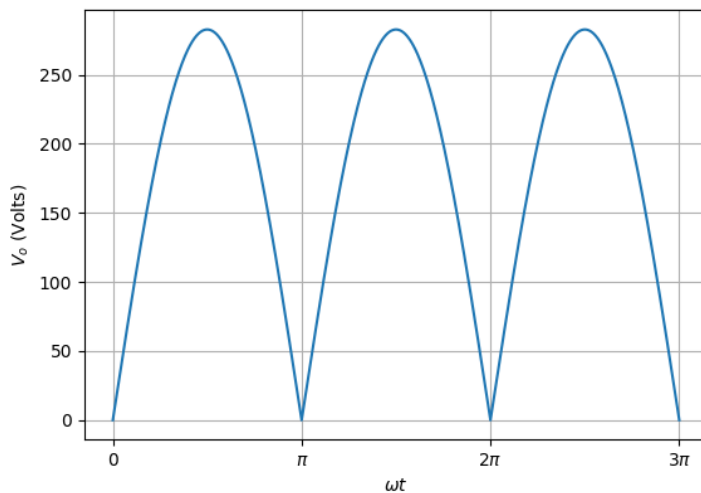


Figure 2. Output voltage waveform of single-phase full bridge rectifier