

GATE:2022 - BM 54

EE23BTECH11025 - Anantha Krishnan


I. QUESTION

A series RLC circuit is connected to 220 V, 50 Hz supply. For a fixed a value of R and C, the inductor L is varied to deliver the maximum current. This value 0.4A and the corresponding potential drop across the capacitor is 330 V. The value of the inductor L is ? (Rounded off to two decimal places).

Solutions :

Symbols	Description	Values
V_s	Input voltage	220 V and 50Hz
χ_L	Impedance across inductor	$j\omega L$
χ_C	Impedance across capacitor	$\frac{-j}{\omega C}$
Z	Impedance across the entire circuit	$R + j\omega L + \frac{-j}{\omega C}$

TABLE I
PARAMETERS, DESCRIPTIONS, AND VALUES

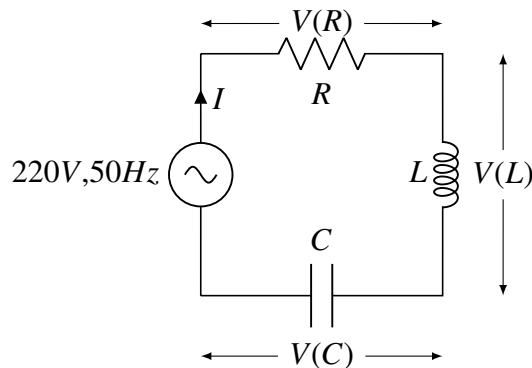

During maximum current $|Z|$ is minimum .

$$I = \frac{V_s}{Z} \quad (1)$$

$$= \frac{V_s}{R + \chi_L + \chi_C} \quad (2)$$

$$= \frac{V_s}{R + j\omega L + \frac{1}{j\omega C}} \quad (3)$$

$$|I| = \frac{|V_s|}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}} \quad (4)$$

Varying L for maximum value of I :

$$\omega L = \frac{1}{\omega C} \quad (5)$$

Putting in (3):

$$I_{max} = \frac{V_s}{R} \quad (6)$$

I_{max} has same phase as V_s (Assume $\angle\phi$). For impedance across the capacitor :

$$V_C|_{I=I_{max}} = I_{max}\chi_C \quad (7)$$

$$-330\angle(90 + \phi) = (0.4\angle\phi)\chi_C \quad (8)$$

$$-330\angle 90 = 0.4\chi_C \quad (9)$$

$$\Rightarrow \chi_C = -825j\Omega \quad (10)$$

For value of Capacitor and inductor, using (5) :

$$L = \frac{825}{100\pi}H \quad (11)$$

$$\approx 2.63H \quad (12)$$

$$C = 3.858 * 10^{-6}F \quad (13)$$

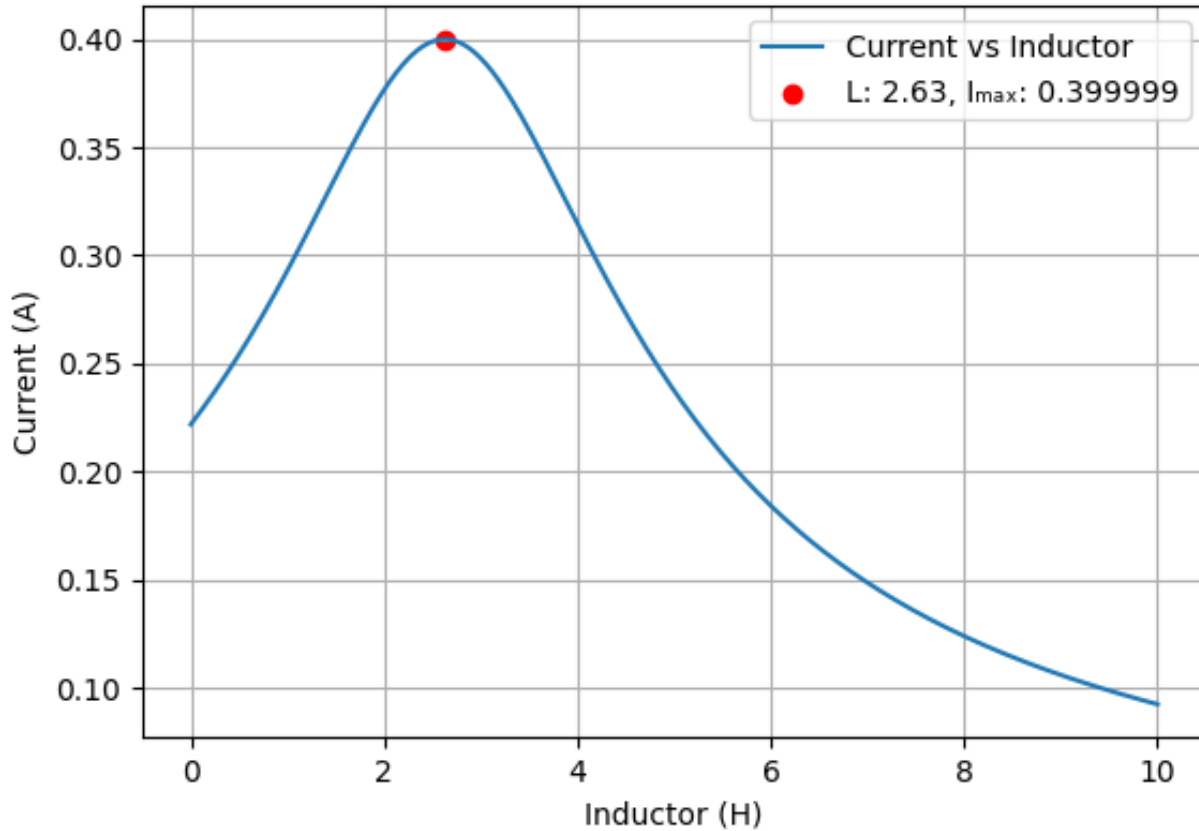


Fig. 1. I vs L