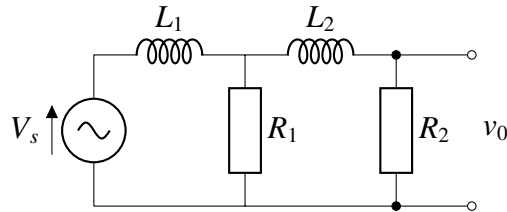


# BM 43

EE23BTECH11048-Ponugumati Venkata Chanakya\*

**QUESTION:** In the circuit shown below,  $R_1 = 2\Omega$ ,  $R_2 = 1\Omega$ ,  $L_1 = 2$  h, and  $L_2 = 0.5$  H. Which of the following describe(s) the correct characteristics of the circuit ?




- 1) Second order high pass filter
- 2) Second order low pass filter
- 3) Under damped system
- 4) Overdamped system

GATE BM 2021

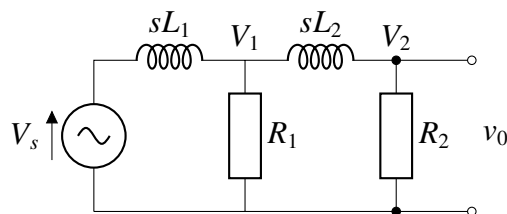**Solution:**

Converting above circuit to frequency domain using laplace transform  
let  $V_1$  and  $V_2$  be voltages at shown positions



Variable	Value
$R_1$	$2\Omega$
$R_2$	$1\Omega$
$L_1$	$2$ H
$L_2$	$0.5$ H

TABLE 4

INPUT PARAMETERS

$$V_0 = V_1 \left( \frac{R_2}{R_2 + sL_2} \right) \quad (1)$$

$$V_1 = V_s \left( \frac{R_1 \left( \frac{sL_2 + R_2}{R_1 + R_2 + sL_2} \right)}{sL_1 + R_1 \left( \frac{sL_2 + R_2}{R_1 + R_2 + sL_2} \right)} \right) \quad (2)$$

$$V_1 = V_s \left( \frac{2 + s}{(2 + s) + s(6 + s)} \right) \quad (3)$$

$$V_0 = V_s \left( \frac{2}{s^2 + 7s + 2} \right) \quad (4)$$

$$\text{let } s = j\omega \quad (5)$$

$$V_0 = V_s \left( \frac{2}{-\omega^2 + 7j\omega + 2} \right) \quad (6)$$

$$= V_s \left( \frac{4 - 2\omega^2 - 7j\omega}{\omega^4 + 45\omega^2 + 4} \right) \quad (7)$$

For lower frequency  $V_0$  is finite and for higher frequency  $V_0$  is zero

$\therefore$  Second order low pass filter

From 5

$$s^2 + 7s + 2 = 0 \quad (8)$$

$$\text{for } as^2 + bs + c = 0 \quad (9)$$

$$(\text{Damping Factor})\zeta = \frac{b}{2\sqrt{ac}} \quad (10)$$

$$\text{By comparing } \zeta = \frac{7}{2\sqrt{2}} \quad (11)$$

$$\implies \zeta > 1 \quad (12)$$

$\therefore$  Over-damped System

$\therefore$  B,D are correct options