

GATE 2022 IN Q52

EE23BTECH11009 - AROSHISH PRADHAN*

Question: In the circuit shown, the load is driven by a sinusoidal A.C. voltage source $V_1 = 100\angle 0^\circ V$ at $50Hz$. Given $R_1 = 20\Omega$, $C_1 = \left(\frac{1000}{\pi}\right)\mu F$, $L_1 = \left(\frac{20}{\pi}\right)mH$ and $R_2 = 4\Omega$, the power factor is _____ (round off to one decimal place)
(GATE 2022 IN Q52)

\therefore Power Factor:

$$\cos(\phi) = \frac{\text{Re}(Z_{\text{eff}})}{|Z_{\text{eff}}|} \quad (4)$$

$$= \frac{8}{\sqrt{8^2 + 6^2}} \quad (5)$$

$$= 0.8 \quad (6)$$

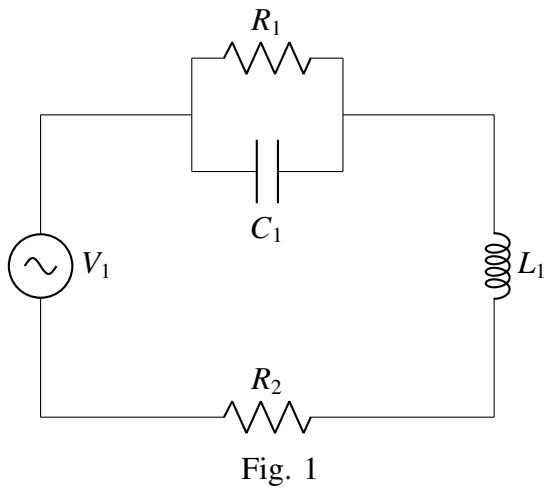


Fig. 1

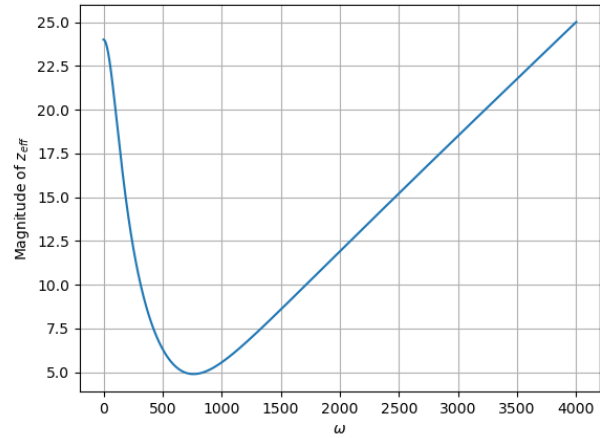


Fig. 2: Plot of Z_{eff} vs ω

Solution:

Symbol	Value	Description
V_1	$100\angle 0^\circ V$	Input Voltage
f	$50Hz$	Frequency
ω	$2\pi f$	Angular Frequency
R_1	20Ω	Resistance
R_2	4Ω	Resistance
C_1	$\left(\frac{1000}{\pi}\right)\mu F$	Capacitance
L_1	$\left(\frac{20}{\pi}\right)mH$	Inductance
Z_{eff}		Impedance
$\cos(\phi)$	$\frac{\text{Re}(Z_{\text{eff}})}{ Z_{\text{eff}} }$	Power Factor

TABLE I: Given Parameters

$$Z_{\text{eff}} = R_2 + j\omega L_1 + \frac{R_1}{R_1 + \frac{1}{j\omega C_1}} \quad (1)$$

$$= 4 + 2j + \frac{-200j}{20 - 10j} \quad (2)$$

$$= 8 - 6j \quad (3)$$